

Question	Answer	Marks	Guidance
1 a i	0.72 (volts) (2)  <b>but if answer incorrect</b>  0.7185 or 0.718 or 0.719 or 0.7 (volts) (1)	2	<b>Allow</b> 0.15 x 4.79 (1)
ii	<b>D</b> (1)	1	if answer line blank allow correct answer circled or underlined  more than one answer = 0 marks
<b>b</b>	<b>Any two from:</b>  increase the current by one from <ul style="list-style-type: none"> <li>- moving the slider clockwise or upwards or to the left</li> <li>- having less wire / fewer coils in circuit [1]</li> </ul> decrease the current by one from <ul style="list-style-type: none"> <li>- moving the slider anticlockwise or downwards or to the right</li> <li>- having more wire / coils in circuit [1]</li> </ul> increasing length increases resistance / increasing resistance decreases current / ORA [1]	2	<b>allow</b> labelled arrows or indications on diagram to indicate correct directions  for upwards <b>allow</b> towards the power supply  for downwards <b>allow</b> away from the power supply  <b>Allow</b> changing length changes resistance [1] <b>But</b> increasing length decreases resistance / ORA [0]  <b>Allow</b> changing resistance changes current [1] <b>But</b> increasing resistance increases current / ORA [0]
	<b>Total</b>	<b>5</b>	

Question	Answer	Marks	Guidance												
2	<p><b>[Level 3]</b> truth table all correct <b>AND</b> An explanation about how logic system is used to display different numbers <b>AND</b> numbers (eg. 2) used to illustrate answer Quality of written communication does not impede communication of the science at this level (5 – 6 marks)</p> <p><b>[Level 2]</b> truth table all correct <b>AND EITHER</b> explanation about how logic system is used to display different numbers <b>OR</b> Numbers (eg. 2) used to illustrate answer Quality of written communication partly impedes communication of the science at this level (3 – 4 marks)</p> <p><b>[Level 1]</b> at least two rows in truth table correct <b>OR</b> explanation about how logic system is used to display different numbers <b>OR</b> numbers (eg. 2) used to illustrate answer Quality of written communication impedes communication of the science at this level (1 – 2 marks)</p> <p><b>[Level 0]</b> Insufficient or irrelevant science. Answer not worthy of credit. (0 marks)</p>	6	<p>This question is targeted at grades up to A.</p> <p>completed truth table:</p> <table border="1" data-bbox="1220 307 1457 451"> <tbody> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table> <p>how his logic system is used to display different numbers may include:</p> <ul style="list-style-type: none"> <li>• Signals / states can be 0 / low / off or 1 / high / on</li> <li>• logic system made of three OR gates and one NOT gate</li> <li>• logic gates work to give different combinations of 0 and 1</li> <li>• when the output / G is 1 then the shaded segment is switched on / ora</li> </ul> <p>numbers to illustrate the answer may include:</p> <ul style="list-style-type: none"> <li>• numbers 1 3 4 5 6 7 8 9 0 need G to be 1 to be correctly displayed</li> <li>• number 2 need G to be 0 to be correctly displayed</li> <li>• numbers 1, 7 and 0 need the <b>middle bar</b> to be 0</li> </ul> <p>Use the L1, L2, L3 annotations in scoris. Do not use ticks.</p>	1	1	1	0	0	0	0	1	1	1	1	1
1	1	1													
0	0	0													
0	1	1													
1	1	1													
<b>Total</b>		<b>6</b>													

Question	Answer	Marks	Guidance			
<b>3</b> <b>a</b> <b>C</b> <b>O</b> <b>M</b> <b>M</b> <b>O</b> <b>N</b>	<table border="1" style="margin-left: 20px;"> <tr><td style="text-align: center;">82</td></tr> <tr><td style="text-align: center;">104</td></tr> <tr><td style="text-align: center;">128</td></tr> </table> <p style="text-align: right;">(1)</p>	82	104	128	1	all correct for 1 mark
82						
104						
128						
<b>C</b> <b>O</b> <b>M</b> <b>M</b> <b>O</b> <b>N</b>	<b>b i</b> $I_b$ is (always much) smaller than $I_c$ / ORA [1]	1				
<b>C</b> <b>O</b> <b>M</b> <b>M</b> <b>O</b> <b>N</b>	<b>ii</b> (idea that) a small base current is needed to switch on the transistor (1)  (this allows) a large current through the transistor (1)	2	<b>allow</b> higher level answers e.g. transistors have a high gain (1)			

Question	Answer	Marks	Guidance
c	<p><b>max two from any of these advantages:</b></p> <p>robot can do jobs that are more: boring / dangerous / unpleasant / intricate / labour intensive / hygienic / take longer</p> <p>Other advantages are that robots are safer / stronger / more efficient / faster</p> <p>Other advantages that robots don't get sick / don't take holidays / don't get paid / don't make human errors / don't take breaks / don't need feeding / don't get tired</p> <p><b>max two from any of these disadvantages:</b></p> <p>robots may be limited in decision making / need reprogramming / expensive to buy or maintain / robots take peoples jobs / may take over (the world) / dangerous to humans if a fault develops (1)</p>	3	<p><b>Ignore</b> can do repetitive work</p> <p><b>Ignore</b> robots do jobs that humans don't want to do</p>
<b>Total</b>		<b>7</b>	

Question	Answer	Marks	Guidance
4 a	<p><b>LDR</b> resistance decreases as light (level) increases / AW [1]</p> <p><b>Thermistor (NTC)</b> resistance decreases as temperature increases / AW [1]</p>	2	<p><b>allow</b> ORA [1]</p> <p><b>allow</b> ORA [1]</p> <p><b>allow</b> heat for temperature</p> <p><b>allow</b> Thermistor PTC resistance increases as temperature increases [1]</p>
b	<p><b>Any two from current passes:</b></p> <p>Idea of threshold voltage reached / AW [1]</p> <p>in one direction / AW [1]</p> <p>when the voltage is positive / resistance is low/AW [1]</p>	2	<p>e.g. if voltage is high enough/ 0.6V</p> <p><b>Allow</b> (the idea that) current is correct direction for the diode [1]</p> <p><b>allow</b> no current when voltage is negative [1]</p> <p><b>allow</b> (idea that) circuit diagram shows diode in forward bias / current direction is L to R / anticlockwise for this diode [1]</p>
<b>Total</b>		<b>4</b>	

Question	Answer	Marks	Guidance															
5 a	<table border="1" data-bbox="361 216 892 539"> <thead> <tr> <th>X</th> <th>Y</th> <th>Z</th> </tr> </thead> <tbody> <tr> <td>(0)</td> <td>(0)</td> <td>1</td> </tr> <tr> <td>(0)</td> <td>(1)</td> <td>0</td> </tr> <tr> <td>1</td> <td>(0)</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table> <p data-bbox="940 577 982 608">[2]</p>	X	Y	Z	(0)	(0)	1	(0)	(1)	0	1	(0)	0	1	1	0	2	<p data-bbox="1121 150 1409 181">all correct for 2 marks</p> <p data-bbox="1121 216 1507 247">2 or 3 rows correct for 1 mark</p>
X	Y	Z																
(0)	(0)	1																
(0)	(1)	0																
1	(0)	0																
1	1	0																
b	<table border="1" data-bbox="472 729 781 1052"> <thead> <tr> <th>E</th> <th>F</th> <th>G</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> </tbody> </table> <p data-bbox="940 1089 982 1121">[2]</p>	E	F	G	0	1	1	0	1	1	0	1	1	1	0	1	2	<p data-bbox="1121 663 1409 694">all correct for 2 marks</p> <p data-bbox="1121 729 1507 760">2 or 3 rows correct for 1 mark</p>
E	F	G																
0	1	1																
0	1	1																
0	1	1																
1	0	1																
<b>Total</b>		<b>4</b>																

Question	Answer	Marks	Guidance
6 a	7.5 (ohms) [2]  <b>but if answer incorrect</b>  correct values of voltage and current from graph [1]	2	correct values e.g. 3 and 0.4 or 6 and 0.8
b	<b>E</b> (no marks)  Idea that longer conductors have a greater resistance [1]  (idea that) the line with the shallowest / least gradient has the greatest resistance [1]	2	If E <b>NOT</b> chosen [0]  Longer length has lower current [1]  allow credit for candidates who calculate the resistance of E as 200 ( $\Omega$ ) [1]
c	<b>mistakes are:</b>  <b>electrons</b> not protons are the charge carriers  atoms vibrate <b>more</b> not less  <b>increases</b> the resistance of the conductor not decreases it	2	<b>allow mistakes indicated on the text</b>  three mistakes corrected [2]  one or two mistakes corrected [1]
<b>Total</b>		<b>6</b>	

Question			Answer	Marks	Guidance
7	(a)	(i)	0.15 (amps) (3)  <b>but if answer incorrect</b>  (I =) $0.75 / 5$ (2)  <b>or</b>  5 or 4.8 to 5.2 (ohms stated as the resistance) (1)	3	<b>allow</b> answer in the range of 0.144 – 0.156 (amps) (3)  <b>allow</b> 5 in range of 4.8 – 5.2  <b>allow</b> 5 (ohms) seen (even in an incorrect calculation) (1) eg. $5 / 0.75$ (1) eg. 5 (taken from graph / slope of graph) (1)
		(ii)	as length increases current reduces / AW / ora (1)	1	<b>allow</b> inversely proportional <b>ignore</b> resistance / faster or stronger current
	(b)		straight line (by eye) on graph starting at / pointing towards (0,0) with a steeper gradient than original line (1)	1	curved line (by eye) scores (0)
<b>Total</b>				<b>5</b>	

Question		Answer	Marks	Guidance
8	(a)	resistance decreases (1) brightness of lamp / current increases (1)	2	<b>ignore</b> weaker resistance <b>ignore</b> faster / stronger current But resistance increases (0) so brightness of lamp / current decreases (1)
	(b) (i)	0.92 ( $\Omega$ ) (2) <b>but if answer is incorrect</b> $\frac{1}{R_T} = \frac{1}{2} + \frac{1}{3}$ (1) <b>or</b> $\frac{1}{R_T} = 0.5 + 0.33 + 0.25$ (1)	2	<b>allow</b> 0.92(307692) (2) <b>allow</b> 0.9 (2) <b>allow</b> $\frac{12}{13}$ ( $\Omega$ ) (2)
	(ii)	4.3 (amps) (2) <b>but</b> $\frac{4}{0.92}$ (1)	2	allow 4.30 to 4.45 (2) allow ecf from bi (2) eg for ecf of 1.08 - allow 3.7 (2) eg for ecf of 9 - allow 0.44 or 0.4 (2) allow 4 / answer to bi (1) eg 4/1.08 (1) <b>allow</b> 4.30 to 4.45 (2) <b>allow</b> $\frac{4}{\text{answer to b(i)}}$ (1)
	(c)	$I_e = 0.60 \text{ mA}$ (1)	1	<b>Allow</b> 0.6 (1)
<b>Total</b>			<b>7</b>	